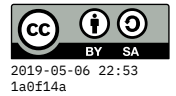


# Boolean logic



## Contents


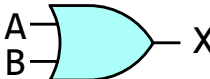
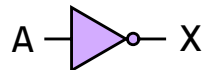
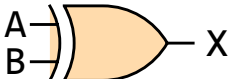
1	Boolean algebra and logic gates	1
2	Combinational circuits	2
3	Sequential circuits	2
4	Logisim software	3
5	Further exploration	4

## 1. Boolean algebra and logic gates

In the 1840s, English mathematician George Boole developed an algebra (a set of operators and laws) for variables that can have just two states – **true** and **false**. Thus, a Boolean value is equivalent to one bit:

False	0	off
True	1	on

The operators defined by Boole are pervasive throughout all of computing. You may have encountered them in doing library or other database searches. The ones we'll consider are:

AND	$X = A \cdot B$	
OR	$X = A + B$	
NOT	$X = A'$	
XOR	$X = A \oplus B$	

The figure illustrates both the algebraic notation and the **circuit diagram** notation. The elements of circuit diagrams are called **gates**, as in “AND gate” or “XOR gate.” The “XOR” ( $\oplus$ ) operator is named for “*exclusive OR*.”


The behavior of these operators can be defined by **truth tables**:

A	B	$A \cdot B$	$A+B$	$A'$	$A \oplus B$
0	0	0	0	1	0
0	1	0	1	1	1
1	0	0	1	0	1
1	1	1	1	0	0

The first two columns indicate the values of the two variables, A and B. There are four rows because two variables can take on four different values ( $2^2 = 4$ ). If there were three variables, there would need to be  $2^3 = 8$  rows.
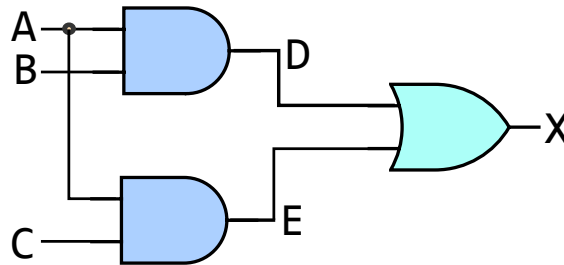
## 2. Combinational circuits

We combine the gates into **combinational circuits** to achieve various effects. For example, the algebraic expression  $X = A \cdot B + A \cdot C$  corresponds precisely to the following circuit diagram:




and we can discover its results by completing the truth table:

A	B	C	$D=A \cdot B$	$E=A \cdot C$	$X=D+E$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

**Exercise:** Try drawing the circuits and the truth tables for  $X = (A \cdot B)'$  and for  $Y = A' + B'$ . They should produce the same result for all inputs A and B. This is one of **DeMorgan's Laws**.

## 3. Sequential circuits

We'll just look at the S-R (NAND) latch.

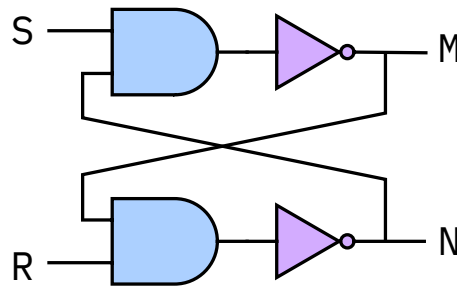

This is a **sequential** circuit, rather than combinational. That means it contains *cycles*. One way to make sense of a cycle is to think in terms of the values of wires *from one moment to the next*. You can subscript each variable with the time of interest:  $S_t$  vs  $S_{t+1}$ , etc.

$$M[t+1] = (S \cdot N[t])'$$

$$N[t+1] = (M[t] \cdot R)'$$

S	R	M[t]	N[t]	M[t+1]	N[t+1]
1	1	1	0	1	0
1	1	0	1	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	0	1	0	1
0	1	0	1	1	1
0	1	1	1	1	0
0	1	1	0	1	0

- Video: Flip Flops, Latches, & Memory<sup>1</sup> from Computerphile [8m53s]

#### 4. Logisim software

This section refers to a program called Logisim<sup>2</sup>, which should run on any platform with a Java Runtime Environment.



Figure 1: On a Mac, if you see the “unidentified developer” error, go **into System Preferences » Security** and look for the button that says **Open Anyway**.

Once you open Logisim, there are a few tools you should familiarize yourself with. The **hand tool** (leftmost on the toolbar) allows you to *turn inputs on and off*. The **arrow**




<sup>1</sup>[youtu.be/-Ecf71b4aZ0](https://youtu.be/-Ecf71b4aZ0)




<sup>2</sup>[www.cburch.com/logisim/download.html](http://www.cburch.com/logisim/download.html)

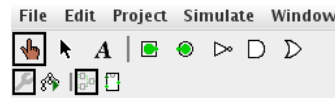**tool** (next to it) allows you to place components onto the grid, move them around, and wire them together.



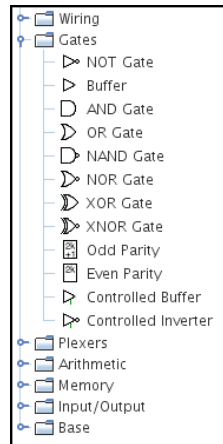In the side-bar, the main components we'll be using are in the **Gates** section, but there's also the **Pin** (under Wiring) and the **LED** (under Input/Output).



When you have a component selected, its properties appear in the lower left of the screen. You can use these to create a label for your pins and LEDs.

Selection: LED	
Facing	North
On Color	#f00000
Off Color	#404040
Active On High?	Yes
Label	Carry
Label Location	East
Label Font	SansSerif Plain 12
Label Color	#000000



<sup>3</sup>[youtu.be/ATPqpFM1Vdw](https://youtu.be/ATPqpFM1Vdw)

Here is the 3-bit adder circuit I did in class. If that file doesn't open automatically in Logisim, you can start Logisim *first* and then use **File » Open**.

- Video: Logisim tutorial<sup>3</sup> from ENGRTUTOR [7m47s]

## 5. Further exploration

- Video: Building a half-adder using dominoes<sup>4</sup>, with Matt Parker on Numberphile [18m30s]
- Video: The big domino adder<sup>5</sup>, demonstrated at the Manchester Science Festival, UK [22m26s]



<sup>4</sup>[youtu.be/lNuPy-r1GuQ](https://youtu.be/lNuPy-r1GuQ)



<sup>5</sup>[youtu.be/0pLU\\_\\_bhu2w](https://youtu.be/0pLU__bhu2w)

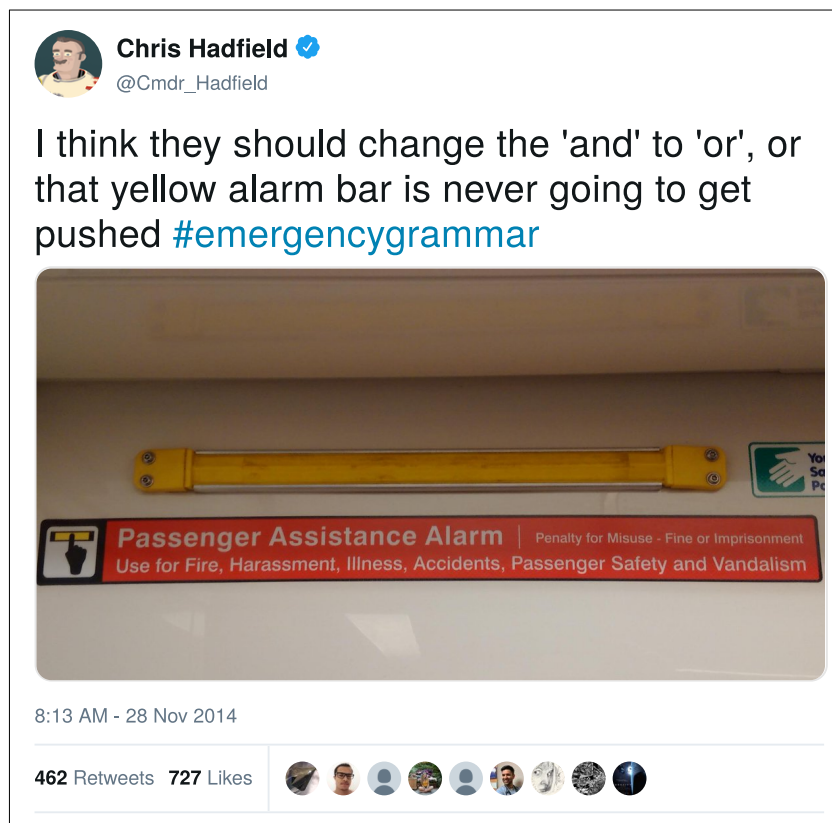


Figure 2: @Cmdr\_Hadfield on Twitter